www.tntextbooks.in

If A = 0 and B = 0 $C=(\bar{0}.\bar{0}) = 1.1 = 1$

If A = 0 and B = 1 $C=(\bar{0}.\bar{1}) = 1.0 = 0$

If A = 1 and B = 0 $C=(\bar{1}.\bar{0}) = 0.1 = 0$

If A = 1 and B = 1 $C=(\bar{1}.\bar{1}) = 0.0 = 0$

Here the truth table is

Input		Output
A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

You can see that, a bubbled AND gate produces the same output as a NOR gate. So, You can replace each NOR gate by a bubbled AN D gate. In other words the circuits are interchangeable.

Therefore

$$\overline{(A + B)} = \bar{A} . \bar{B}$$

Which establishes the De Morgan's first theorem.

2.9.6 NAND Gate

The NAND gate operates an AND gate followed by a NOT gate. It acts in the manner of the logical operation "AND" followed by inversion. The output is "false" if both inputs are "true", otherwise, the output is "true". In otherwords the output of the NAND gate is 0 if and only if both the inputs are 1, otherwise the output is 1. The logice circuit of NAND gate is

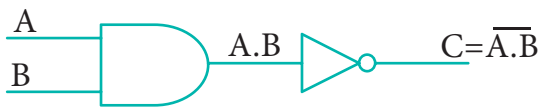

Fig. 2.11 Logic Circuit of NAND Gate

The logical symbol of NAND gate is

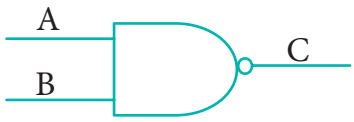

Fig. 2.12 Logic Symbol of NAND Gate

The output of the NAND gate is

$$C = \overline{(A . B)}$$

Read this as "C" equals NOT of A AND B" or "C" equals the complement of A AND B".

For example if both the inputs are 1

$$C = \overline{(1 . 1)} = \bar{1} = 0$$

The truth table for NAND gate is

Input		Output
A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Table 2.11 Truth Table for NAND Gate

2.9.7 Bubbled OR Gate

The logic circuit of bubbled OR gate is

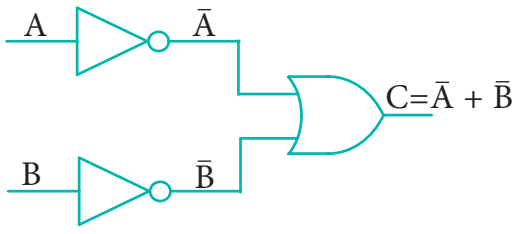

Fig. 2.13 Logic Circuit of Bubbled OR Gate